

64-tap 16-bit FIR filter

Aarya Agarwal
Columbia University
CSEE W4823
New York, New York
asa2276@columbia.edu

Stephen Ogunmwonyi
Columbia University
CSEE W4823
New York, New York
iso2107@columbia.edu

Abstract—This document discusses our design and implementation of a 64-tap 16-bit FIR filter for “Advanced Logic Design” (W4823) at Columbia University

I. INTRODUCTION (HEADING I)

A 16-bit 64-tap FIR (Finite Impulse Response) filter is a type of digital filter used in signal processing that operates with 16-bit precision and processes input data using 64 filter coefficients, or "taps," to produce its output. It works by applying a weighted sum of the current and previous input samples, allowing it to perform tasks such as noise reduction, signal smoothing, and frequency shaping with high accuracy. This computation is also referred to as a discrete convolution. Common applications include audio signal processing, communication systems (like equalization and channel filtering), and biomedical signal analysis (e.g., ECG filtering).

$$y[n] = \sum_{i=0}^N b_i \cdot x[n-i]$$

$x[n]$ is the input signal, $y[n]$ is the output signal,
 N is the filter order (number of taps), b_i is the
filter coefficient

Fig. 1. FIR Filter formula

II. DESIGN

A. Controller

This controller ASM diagram describes the operation of a 64-tap FIR filter. The process starts by loading the coefficients and input data, then initializes counters and output values. For each iteration, the filter computes the output as a sum of the product of coefficients and input values, incrementing counters until all 64 taps are processed, after which it shifts the values and repeats the process.

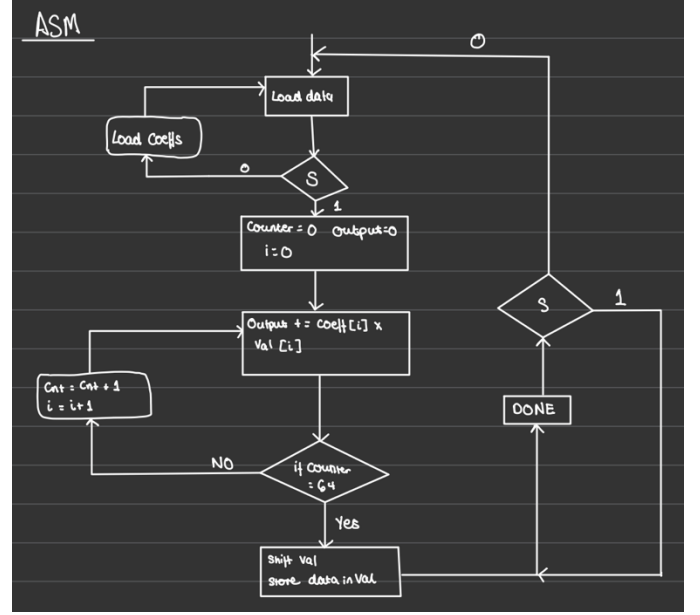


Fig. 2. FIR Filter controller ASM diagram

B. Datapath

This datapath block diagram shows the interaction between a FIFO, IMEM, SRAM, and an ALU for processing data. The FIFO stores incoming data, providing inputs to the IMEM Shift Register, which handles read and load operations before passing data to the ALU. The SRAM Coefficient Memory supplies coefficients to the ALU for computations, with signals like chip enable (CEN) and write enable (WEN) managing access. The ALU processes inputs, performs operations based on the opcode, and sends the results back through a multiplexer (MUX) and a register, completing the computational cycle.

 


Fig. 6. FIFO post-synthesis waveforms

IV. RUNTIME ANALYSIS

A. Output

Our FIR filter takes in input via the hardcodes found in our testbench “test_tb_modified.” In our testing, we also created the following monitor in our controller/datapath module “test.v,” which obviously has to be commented out in order for synthesis, which is why in synthesis there is greater reliance on the waveforms.

 


Fig. 7. FIR post-synthesis signals initializing

 


Fig. 8. FIR post-synthesis output signals and calculations

# Time=6673500000	tapIndex=10	currentSum=1034	aluResult=160	sum=866	result=866
# Time=6673501000	tapIndex=10	currentSum=1034	aluResult=212	sum=866	result=866
# Time=6674500000	tapIndex=11	currentSum=1246	aluResult=203	sum=1034	result=1034
# Time=6674501000	tapIndex=11	currentSum=1246	aluResult=254	sum=1034	result=1034
# Time=6675500000	tapIndex=12	currentSum=1500	aluResult=244	sum=1246	result=1246
# Time=6675501000	tapIndex=12	currentSum=1500	aluResult=38	sum=1246	result=1246
# Time=6676500000	tapIndex=13	currentSum=1538	aluResult=27	sum=1500	result=1500
# Time=6676501000	tapIndex=13	currentSum=1538	aluResult=76	sum=1500	result=1500
# Time=6677500000	tapIndex=14	currentSum=1614	aluResult=64	sum=1538	result=1538
# Time=6677501000	tapIndex=14	currentSum=1614	aluResult=112	sum=1538	result=1538
# Time=6678500000	tapIndex=15	currentSum=1726	aluResult=99	sum=1614	result=1614
# Time=6678501000	tapIndex=15	currentSum=1726	aluResult=146	sum=1614	result=1614
# Time=6679500000	tapIndex=16	currentSum=1872	aluResult=132	sum=1726	result=1726
# Time=6679501000	tapIndex=16	currentSum=1872	aluResult=178	sum=1726	result=1726
# Time=6680500000	tapIndex=17	currentSum=2050	aluResult=163	sum=1872	result=1872
# Time=6680501000	tapIndex=17	currentSum=2050	aluResult=208	sum=1872	result=1872
# Time=6681500000	tapIndex=18	currentSum=2258	aluResult=192	sum=2050	result=2050
# Time=6681501000	tapIndex=18	currentSum=2258	aluResult=236	sum=2050	result=2050
# Time=6682500000	tapIndex=19	currentSum=2494	aluResult=219	sum=2258	result=2258
# Time=6682501000	tapIndex=19	currentSum=2494	aluResult=6	sum=2258	result=2258
# Time=6683500000	tapIndex=20	currentSum=2500	aluResult=244	sum=2494	result=2494
# Time=6683501000	tapIndex=20	currentSum=2500	aluResult=30	sum=2494	result=2494
# Time=6684500000	tapIndex=21	currentSum=2530	aluResult=11	sum=2500	result=2500
# Time=6684501000	tapIndex=21	currentSum=2530	aluResult=52	sum=2500	result=2500
# Time=6685500000	tapIndex=22	currentSum=2582	aluResult=32	sum=2530	result=2530
# Time=6685501000	tapIndex=22	currentSum=2582	aluResult=72	sum=2530	result=2530
# Time=6686500000	tapIndex=23	currentSum=2654	aluResult=51	sum=2582	result=2582
# Time=6686501000	tapIndex=23	currentSum=2654	aluResult=90	sum=2582	result=2582
# Time=6687500000	tapIndex=24	currentSum=2744	aluResult=68	sum=2654	result=2654

Fig. 9. FIR pre-synthesis monitor

B. Performance

Our design met slack and the following results are based on the pt results obtained.

Throughput: 22 [kS/s]

Maximum clock frequency: 1 MHz (Could potentially get faster with some tweaking of pipelining)

Total Power: 16uW

Max power: 0.2889 W

Area: 102245.77 um²

Accuracy: Worst case: 0% | Average: 98.4%